

Microchip Morse Decoder

Very many amateur shacks are now equipped with some sort of computer, and morse reading programs are readily available for most of the popular types. A

sending is displayed as a space, and any unrecognisable characters are displayed as an asterisk. Word wrapping is prevented by printing a CR/LF sequence if a space is

memory (RAM) is provided. This is unusual, but the Z80 itself contains sufficient register storage for our needs, provided that certain restrictions are understood. Firstly, there can be no PUSH or POP's to the stack. There can be no stack without RAM! Secondly, no subroutines may be used, since without a stack there is nowhere to store the return address. Similarly interrupts cannot be used, though this does release the I register for other purposes. In fact a trick method of calling subroutines is used, as follows:

A nifty gadget to decode and print morse (via a Centronics printer) from Phil Green, G4PHL.

disadvantage of using the home micro in this way is that the machine is fully occupied for long monitoring periods, preventing its use for other purposes. Few machines offer true multi-tasking, so the morse reader must be interrupted if any locator, bearing, or logging programs need to be run. By the time a station has been located and the beam set up accordingly, the contact may well have finished.

This circuit can be regarded as a simple morse-to-centronics converter which releases the main station computer for more interesting tasks, and gives a hard-copy printout for later perusal. The circuit hardware is based on an idea from the Zilog handbooks, this being the simplest Z80 implementation imaginable. Comprising of only four chips, it is a well tried and tested circuit with the benefit of having very little to go wrong. Constructors with little experience in microprocessors can approach this project with confidence, especially since all the chips used have been seen on sale at various rallies for a fraction of the normal retail price. Never pay more than 50p for a Z80!

Operation

When the power is first applied, the power-on-reset operates and the title "Morse to Centronics converter" is displayed on the printer. If good morse is then applied to the port A input, using a logic low for tone, and logic high for no tone, the decoded text will be printed out. A pause in

decoded after the 70th character typed (the interrupt page register is used for this count!).

The software can track accurately between about 8 to 24 wpm, but as in any decoding program, does need reasonable quality morse. It can therefore be usefully employed as a training aid by attaching a practise key to the input. All alphabetic characters, numbers, and punctuation signs are catered for as well as the barred procedural characters.

System Considerations

A glance at the memory-map will reveal that no read-write

```
LD IY,$+7 ; IY holds return
                address
JP SUB        ; call the subroutine
//           ; next instruction...
//
```

The subroutine itself would be arranged as follows:

```
//           ; code...
//           ; ... code
JP (IY)       ; Pseudo return
                instruction
```


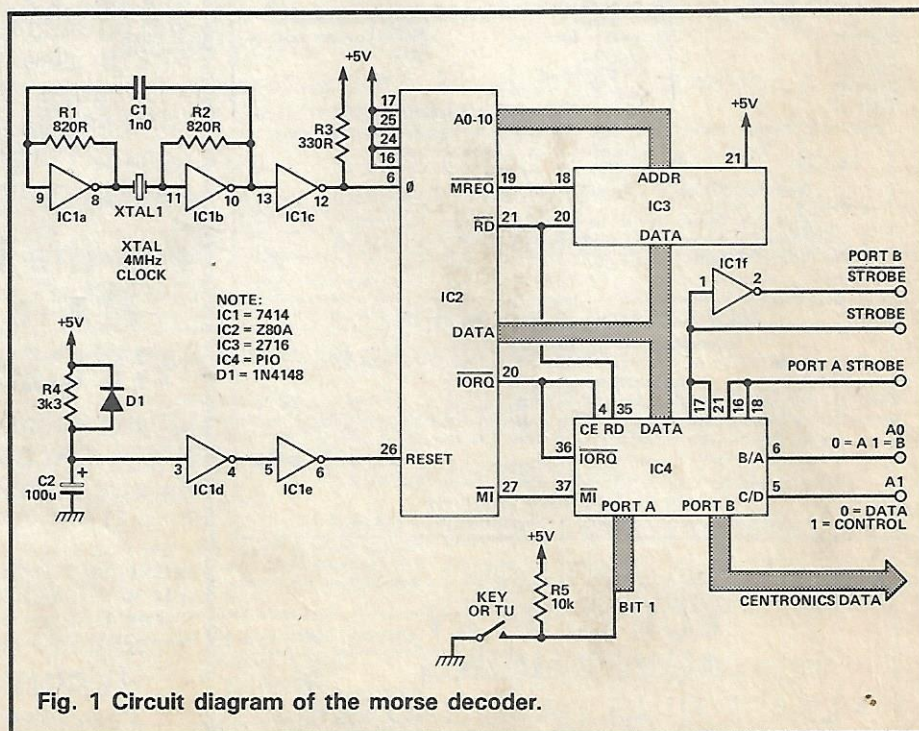


Fig. 1 Circuit diagram of the morse decoder.

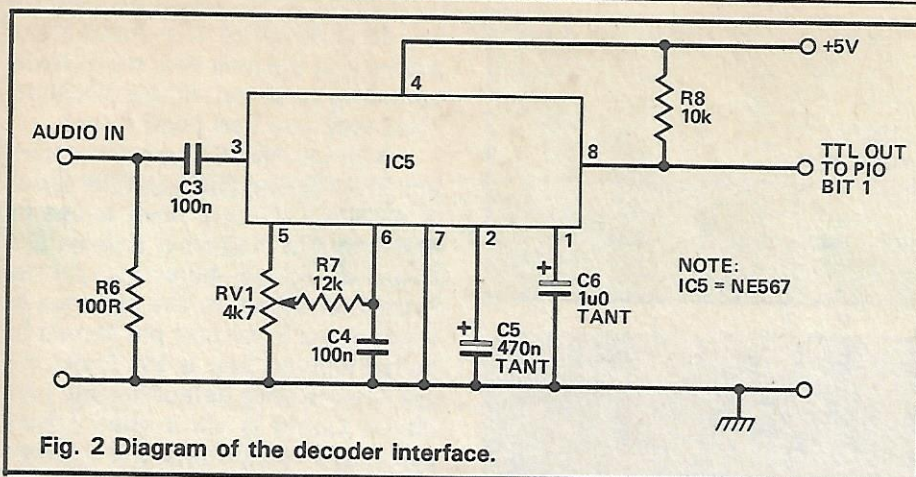

Provided the IY register is not used during the subroutine, this works fine. Remember we cannot PUSH IY to save it!

Construction

The four IC's used are the Z80 itself, a parallel input/output chip, a 2716 EPROM containing the morse reading software, and a 7414 TTL chip which provides the 4MHz clock and power-on reset.

Veroboard was used for all of the prototypes, however almost all the

tracks are cut adjacent to each IC pin, interconnections being individually wired. The physical layout of the board is not at all critical, and could be made a little larger if required. Wiring should follow the table provided, veropins being used for the power connections. Where two connections are made to one pin, for example the data lines and address lines 0 and 1, it is easier to thread two wires through first before soldering. Lay all the wiring neatly between the IC's rather than taking the shortest route between two pins.

0000	3E	4F	D3	02	3E	0F	D3	03	AF	ED	47	21	A8	A1	7E	23
0010	B7	28	0C	D3	01	11	00	18	1B	7A	B3	20	FB	18	EF	3E
0020	14	47	0E	01	21	00	00	FD	21	2E	A0	C3	E5	A0	30	40
0030	24	7C	CB	3F	CB	3F	CB	3F	B8	38	0B	FD	21	42	A0	C3
0040	E5	A0	30	DB	18	F5	FD	21	4D	A0	C3	E5	A0	38	E1	2C
0050	78	CB	3F	BD	38	10	FD	21	5D	A0	C3	E5	A0	30	F0	7C
0060	85	67	2E	00	18	CA	7C	CB	3F	B8	CB	11	26	00	18	09
0070	2C	7D	CB	3F	CB	3F	B8	30	20	FD	21	80	A0	C3	E5	A0
0080	30	EE	24	78	CB	3F	BC	38	42	FD	21	90	A0	C3	E5	A0
0090	38	F0	7D	8C	6F	26	00	18	D7	79	FE	01	28	16	FD	21
00A0	A5	A0	C3	07	A1	11	00	0C	1B	7A	B3	20	FB	FD	21	B4
00B0	A0	C3	07	A1	2E	00	26	00	FD	21	BF	A0	C3	E5	A0	30
00C0	F5	24	78	CB	3F	BC	30	F0	C3	46	A0	78	CB	3F	80	BD
00D0	38	07	78	85	CB	3F	47	18	07	FD	21	E0	A0	C3	07	A1
00E0	2E	00	C3	46	A0	50	59	06	05	0E	00	DB	00	E6	02	81
00F0	4F	D9	08	01	8E	00	0B	78	B1	20	FB	08	D9	0F	10	EB
0100	79	FE	06	42	4B	FD	E9	79	D9	01	32	00	21	40	A1	ED
0110	B1	01	31	00	09	7E	D3	01	D9	ED	57	3C	ED	47	79	FE
0120	01	20	19	ED	57	FE	46	38	13	3E	0D	D3	01	11	00	0C
0130	1B	7A	B3	20	FB	3E	0A	D3	01	AF	ED	47	0E	01	FD	E9
0140	01	06	17	15	0B	03	1D	09	1F	07	18	0A	1B	04	05	08
0150	19	12	0D	0F	02	0E	1E	0C	16	14	13	30	38	3C	3E	3F
0160	2F	27	23	21	20	2E	6A	2D	4C	35	BA	7A	73	47	2A	52
0170	29	00	20	41	42	43	44	45	46	47	48	49	4A	4B	4C	4D
0180	4E	4F	50	51	52	53	54	55	56	57	58	59	5A	31	32	33
0190	34	35	36	37	38	39	30	3D	2E	2F	2C	40	2D	21	3F	3A
01A0	3E	29	3C	2A	00	00	00	00	47	34	50	48	4C	20	4D	6F
01B0	72	73	65	20	74	6F	20	43	65	6E	74	72	6F	6E	69	63
01C0	73	20	43	6F	6E	76	65	72	74	65	72	2E	20	20	38	2D
01D0	32	34	20	57	50	4D	2E	0D	0A	0A	00	FF	FF	FF	FF	FF
01E0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF
01F0	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF	FF

Fig. 3 Hexadecimal listing of the EPROM contents.



Insert the 7414 first, apply power, and listen for the 4MHz clock or a harmonic on your communications receiver, to confirm operation. When inserting the larger chips, be careful not to bend any pins under the chip.

The input/output connectors were fashioned from 16 pin turned DIL sockets, by cutting them to form two eight-way strips. These can be conveniently mounted directly alongside the PIO. Suitable plugs can be made in a similar manner by cutting a 16 pin header.

An alternative to Veroboard is the specially designed PCB, available through our Reader Services Department. Details of how to order it are available at the end of the article.


It is important the IC sockets are used for projects like this one since this encourages experimentation and allows for the occasional "blow-up" without too much disappointment. Junk box and surplus components can be tested on the board without risk of damaging anything expensive.

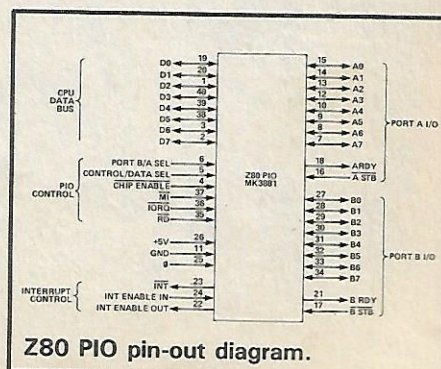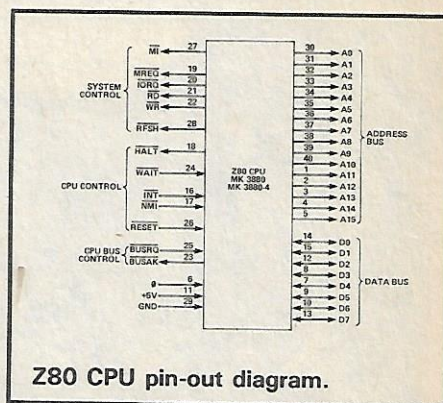4MHz crystals were used in all the prototypes since these were to hand, however 3.579MHz colour burst crystals would probably suffice giving a reduced speed coverage of say 7 to 20 WPM without altering the software. If this is acceptable then by all means use them and save a little. 4.433MHz British colour crystals may work equally well for




Memory and I/O Map

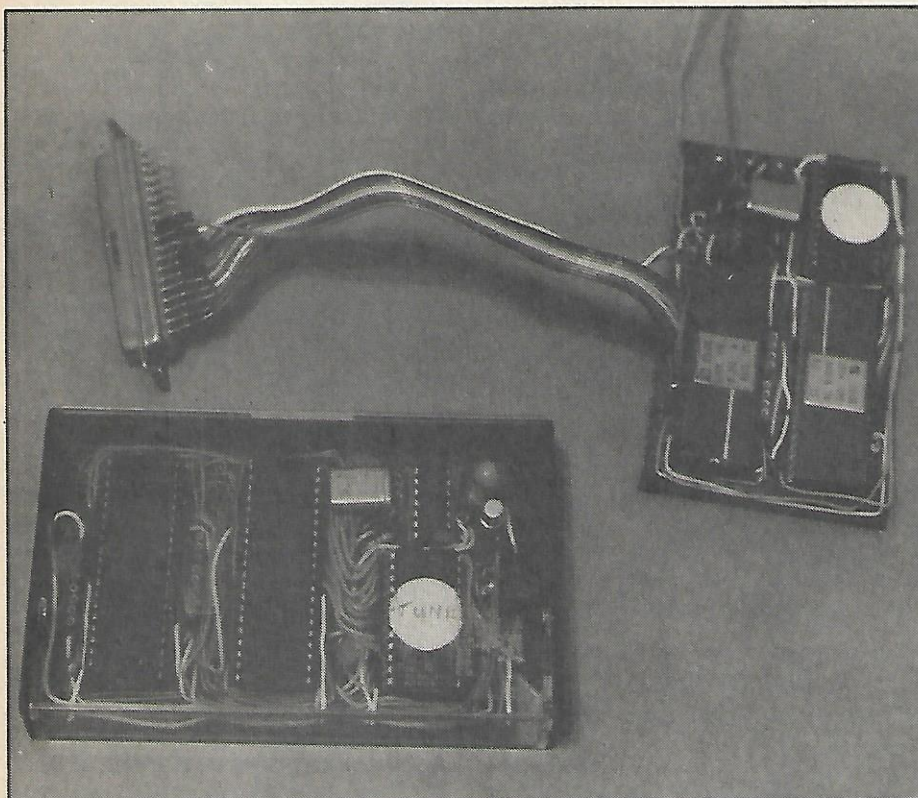EPROM: 0000 — 07FF reflected at 2k intervals
I/O 00 — 03 reflected at 4 byte intervals
PORT A: data — 00 software configured for key or TU input
 control — 02
PORT B: data — 01 software configured for Centronics output
 control — 03



Photos of the prototype decoder boards.

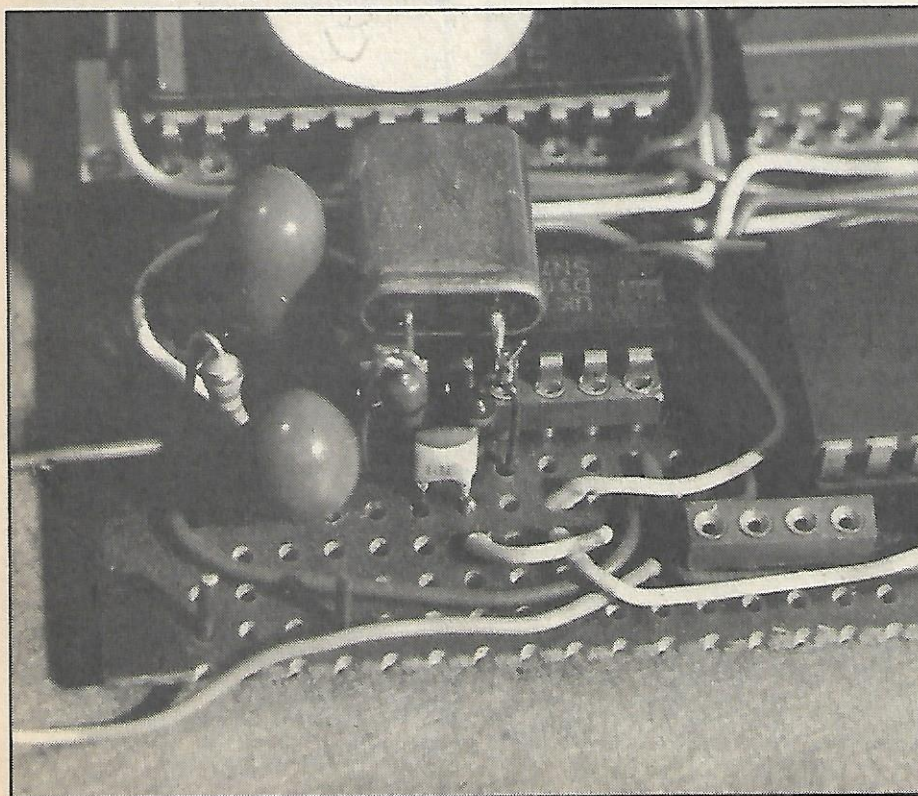

say 10 to 30 WPM. If in doubt about a crystal in the junk box, try it! Avoid spending a lot on simple projects. That way you can build more!

A simple NE567 type of terminal unit is sufficient, and a sample circuit is provided. Others have appeared elsewhere in magazine articles and there is scope here for further experimentation. In the absence of a signal the input port pin should be pulled high by, say, a 10k resistor if the TU does not default to this condition. Output is via a ribbon cable carrying 8 bits of data and a strobe signal. No busy signal is required from the printer due to the limited speed requirements.

Other Uses

The board will adapt very easily to other uses simply by changing the EPROM, and has been used, among projects, as an RS232 to Centronics converter (and vice versa), a code converter, a musical box, an EPROM blower interface and a musical doorbell. The author can supply details of the software that is available if you send him an SAE at the address given below. Don't be frightened of microprocessors and associated chips, or regard them as useful only within a computer. They are after all only components, and cheap and readily available components at that!

EPROMs may be programmed from the hex listing shown, or pre-programmed EPROMs may be purchased from the author for £3 each at: 6 Yews Close, Worrall, Sheffield S30 3BB.

The author would like to thank Geoff Taylor, G4KPU, for building the second prototype, and Stewart Ward, G6BCM, for photographing both prototypes.

Special PCB

The PCB for this project is available from our readers services department, price £9.40 including VAT and P&P. Orders should be sent to: Argus Specialist Publications Ltd, Readers' Services, 9 Hall Road, Hemel Hempstead, Herts HP2 7BH. Credit card orders can be placed on 0442 211882 (office hours only, for the present). Please remember to quote the board reference number, which is R8701-1, or you're liable to get the wrong PCB! Please allow up to 28 days for delivery.

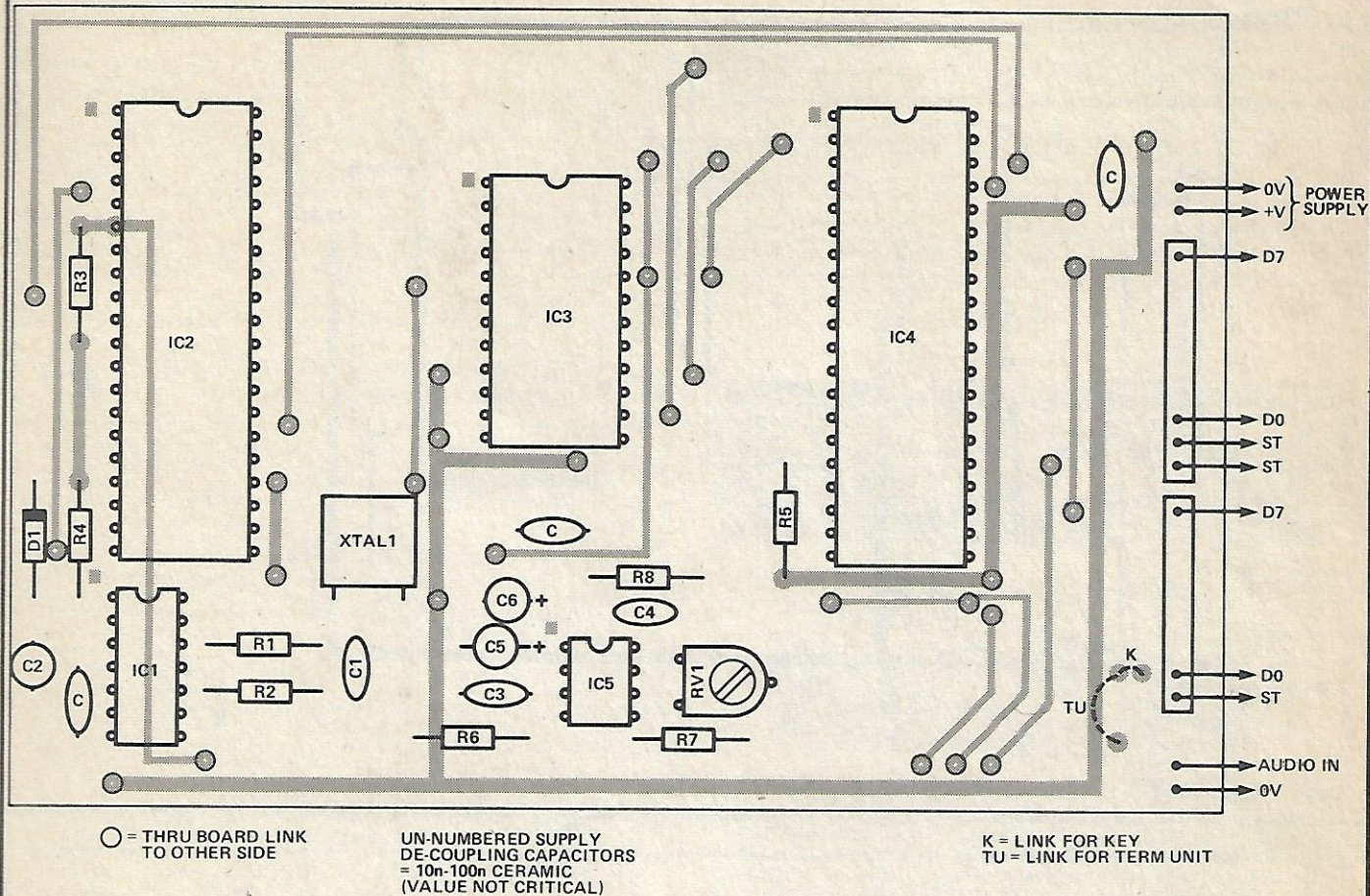


Fig. 4 Component placement for the decoder

Components List

RESISTORS

R1,2	820R
R3	330R
R4	3k3
R5,R8★	10k
R6★	100R
R7★	12k
RV1★	4k7 preset potentiometer

CAPACITORS

C1	1n0
C2	100u 12V electrolytic
C3★,C4★	100n
C5	470n tantalum
C6	1u0 tantalum

SEMICONDUCTORS

IC1	7414
IC2	Z80A CPU
IC3	2716 programmed EPROM
IC5★	NE567
IC4	280PIO
D1	1N4148

MISCELLANEOUS

XI 4MHz (or close) crystal
Centronics printer plug; circuit board (PCB or stripboard); wire, etc.

★ Denotes an item used in the terminal unit — may be omitted if not required.

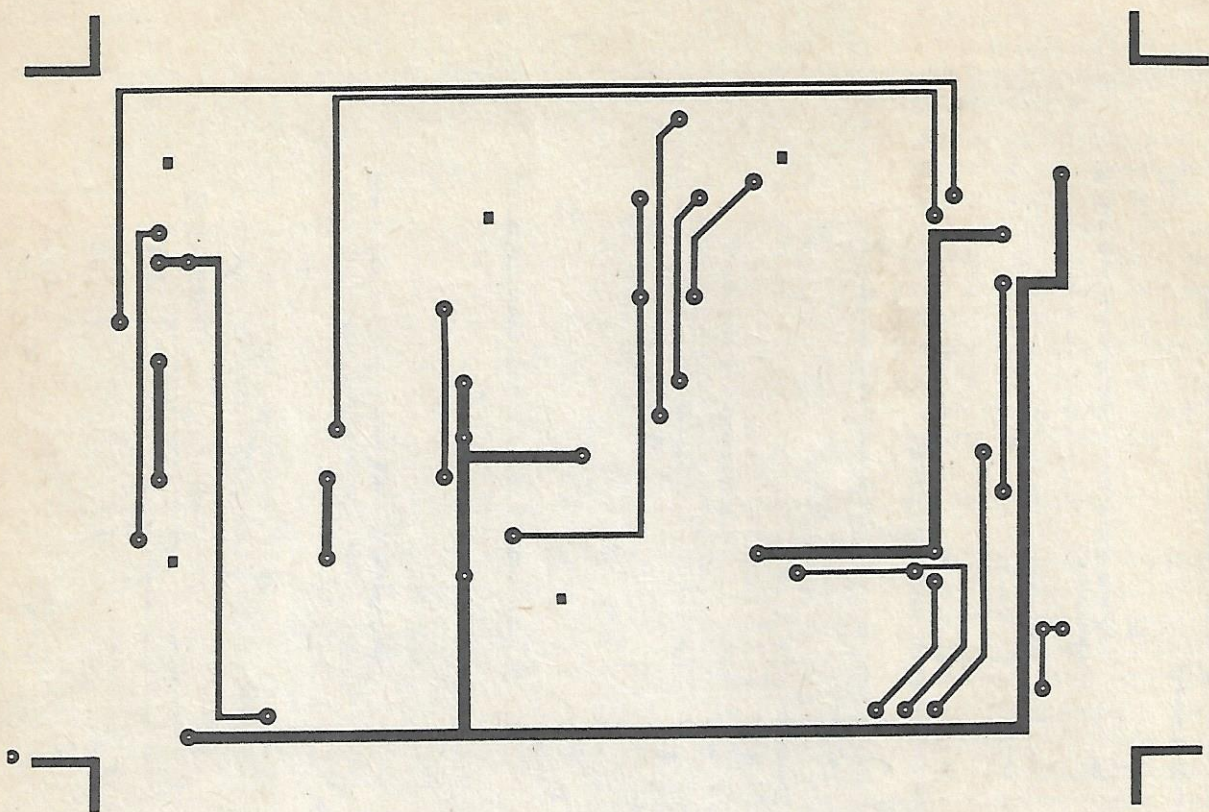


Fig. 5 Topside PCB track layout (full size).

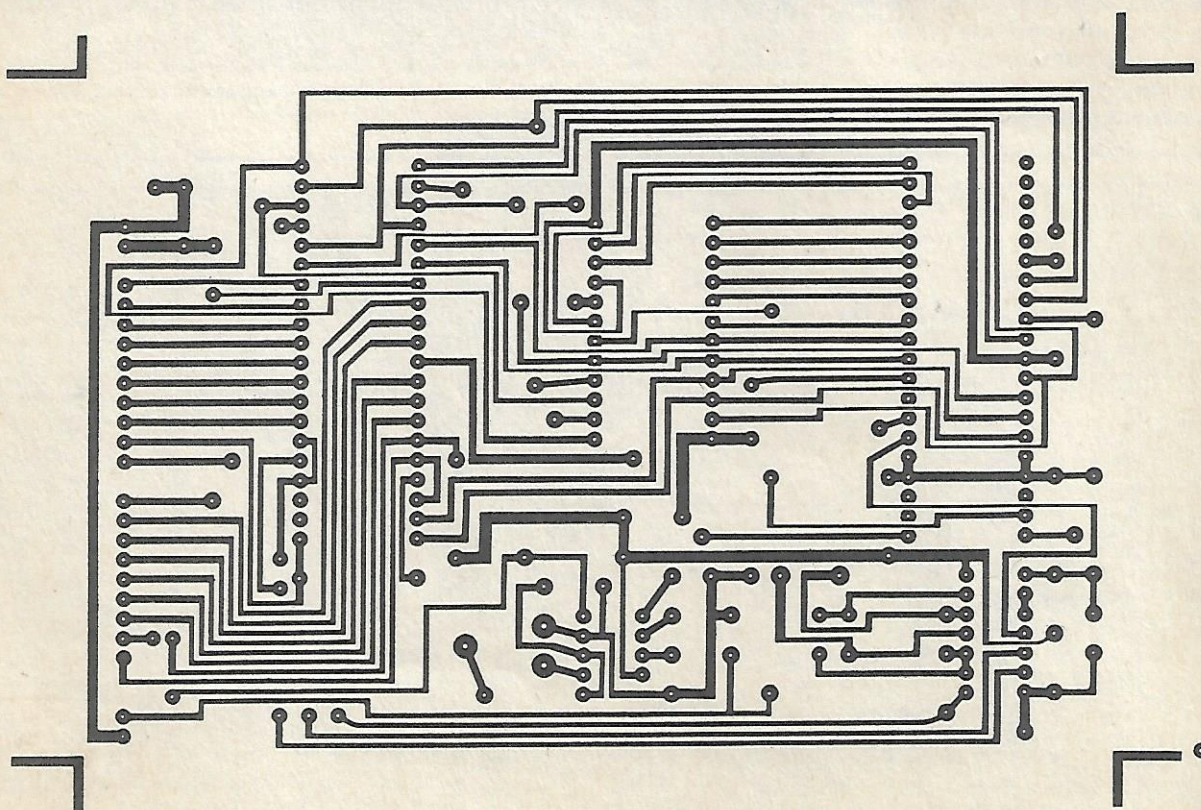


Fig. 6 Underside PCB layout (full size).

UPDATE·MICROCHIP MORSE DECODER

By adding a plug-in selector switch and a changing of EPROM program, the HRT Z80 decoder board (described in the January 1987 edition) can be made to decode several additional modes other than Morse code.

The Morse software is very compact at well under half a kilo byte, and there is ample room in the 2716 EPROM for an additional RTTY and ASCII receive option. Selection of the required mode is done by reading port A, which is configured by the software to give 8 inputs. A simple switch to ground on each input and a pull-up resistor of about 1 to 10k are all that are required. This can be built conveniently on a small piece of stripboard, using an eight-way DIL switch (which can be socket mounted if preferred), an in-line resistor pack, and a plug made from a 16 pin DIL header.

***Phil Green, G4PHL,
adds a few ASCII bells
and RTTY whistles to the
Morse to Centronics
decoder.***

A change of mode requires a reset or power off-on cycle, since port A is not continuously monitored by the program. After a reset, the new mode, clock rate and baud rate

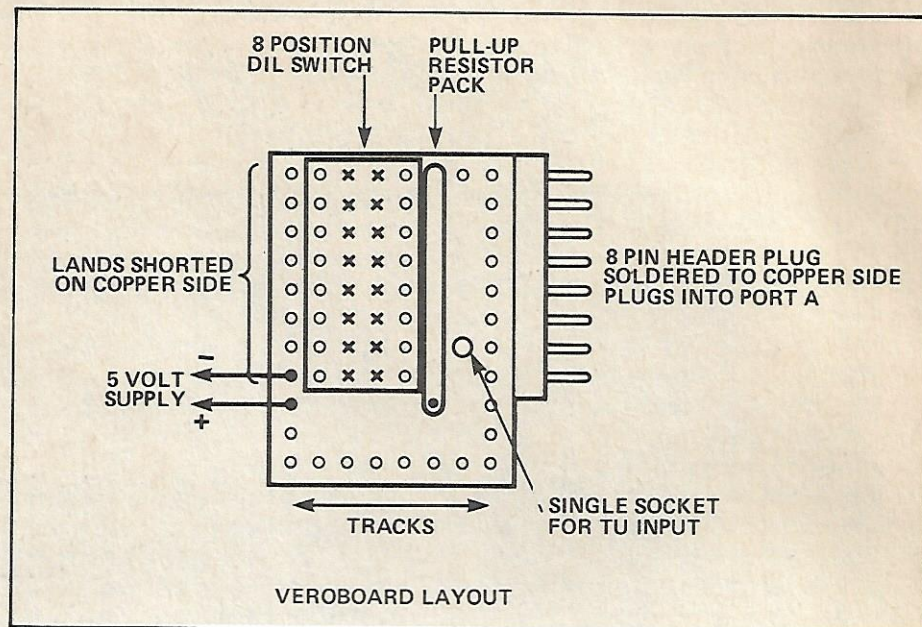


Fig. 2 A possible layout for the switches and resistors.

will be printed for reference. Note that since the TU input is to bit one (not zero!), no switch is needed on this pin.

The allocation of port A bits is shown in the Table. One of the switches allows the timing dependant routines to be adjusted to suit either a 3.579 or 4.000MHz clock oscillator crystal, allowing the most convenient crystal to be used. Bit zero (SW1) is unused, as is mode selection 4, and I hope that anyone with an interest in programming who produces a program for the board,

will write to HRT so that we can produce a pool of useful software to be shared with other readers.

The Terminal Unit

Much time has been spent trying to get reliable operation out of the built-in NE567 terminal unit on RTTY and ASCII. Unfortunately, it has proved barely adequate, as it was intended as a cost effective way to interface Morse only. However, with a little experimentation it is possible to get something out of it, although the author would recommend use of the ST5 TU with TTL output for consistent results.

An external TU is certainly necessary for ASCII as this uses CUTS tones (1200/2400Hz) at 300 baud. Standard tone frequencies used for RTTY are 1445Hz for mark (the standing condition when no information is being transmitted) and 1275Hz for a space. The on-board terminal unit can detect only one of the two RTTY tones, assuming that if one tone is absent, the other must be present. It cannot perform as well as, say, the ST5 or similar, but works pretty well on CW. Noisy HF signals are bound to cause trouble, unless some filtering is added.

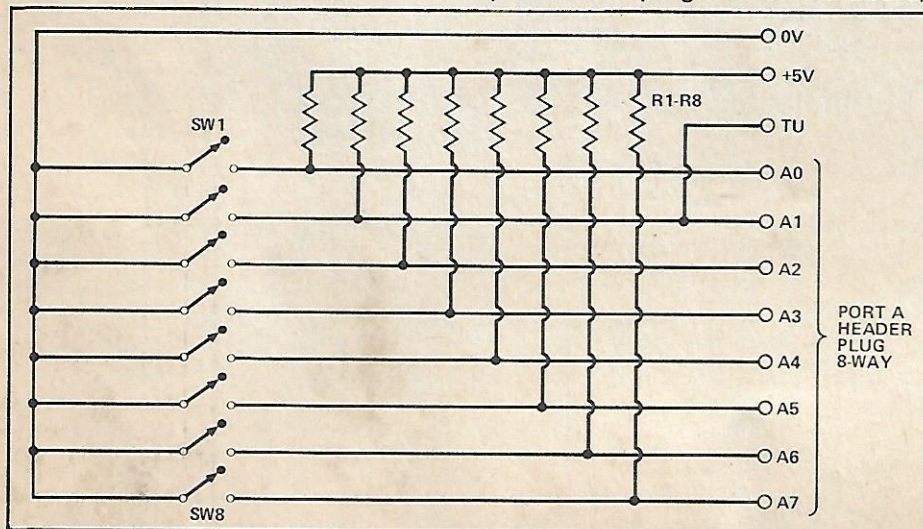


Fig. 1 The resistors and switches needed to access the alternative modes.

The bandwidth of the NE567 is set by C5 on pin 2, and some experimentation here may give an improvement. Generally the higher the capacitance, the tighter the bandwidth. RTTY frequencies can be easily achieved by replacing resistor R7 (12k) with one of 4k7. In this case, the NE567 should be tuned to the lower pitched RTTY tone, 1275Hz. During a mark condition therefore the NE567 output will be high (out of lock, no tone detected), and during a space condition the NE567 will lock and drive its output low.

RV1 should be carefully set to tune the TU to 1275Hz, using either a counter on pin 5, or alternatively by beating pin 5 audibly with a known reference tone. Test tones can readily be generated with reasonable accuracy by most personal computers, using the SOUND or PLAY commands. The NE567 output, one for mark, and a zero for space, is then applied to the PIO input bit one as in the Morse code.

Another unknown when tuning an RTTY signal is its baud rate. On the HF amateur bands, 45.5 is the most common, but 50 is the norm for VHF. Most commercial news stations use 50 baud, but there are several at 75. Usually, experience will enable the user to estimate the baud rate by ear. Given the inherent tolerance of the start/stop teleprinter code, however, selection is not as difficult as it sounds!

New Facilities

Baud rates of 45, 50, 56, and 75 are provided on RTTY, and 100 or 300 in ASCII mode (but note that some printers may not be able to

cope with continuous data at 300 baud, there being no 'busy' lead. Automatic unshift-on-space is provided during RTTY reception, to prevent prolonged errors should a figure shift be induced by noise. The Morse software is unchanged from the original January article. Incidentally, the 300 baud to Centronics mode allows computers with only a serial port access to a parallel printer, but using the Microchip Morse Decoder to do this really is taking overkill to the extreme!

Although the baudot to centronics mode will be used mostly for receiving radio-teleprinter signals, it is of course equally happy printing a 'land-line' telex, via a suitable level shifter (an opto-isolator is ideal). The prototypes proved invaluable in this mode, which, although limited to receive only, allows an inconspicuous printer to be located on the office desk for incoming telex calls. Signals are +/- 80 volts at 50 baud from the exchange (mark is -80) and a suitable interface circuit is shown in Fig. 3 since the module and printer are effectively in parallel with the main office teleprinter two paper copies are available.

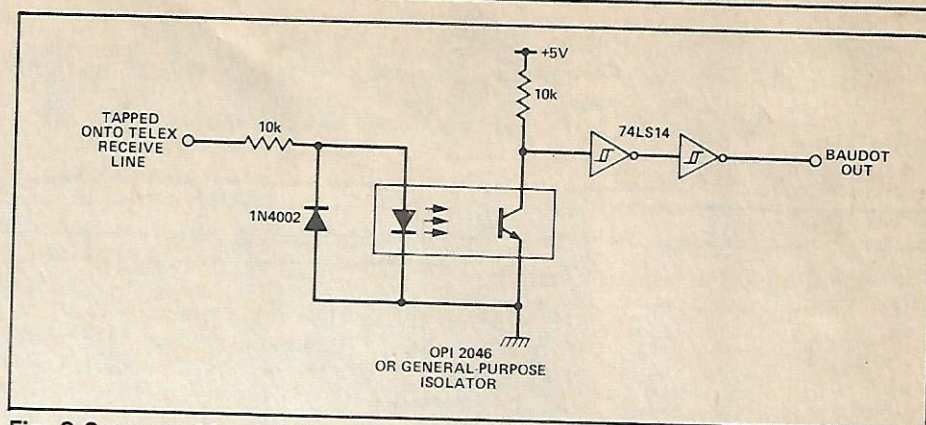


Fig. 3 Suggested level shifter for telex to TTL conversion.

As the reader will appreciate, some considerable work has gone into programming this little unit, and so the new software will be slightly more expensive at £5. For the same reason, no dump of the EPROM contents will be published. Anyone who has the 'Morse only' software can on return of the EPROM, have it updated to multi-code for a charge of £3. These are available from the author at 6 Yews Close, Worrall, Sheffield, S30 3BB.

Gremlins Corner

Three gremlins crept into the original article, which were:

- The 'earthy' end of RV1 shouldn't be earthed at all. Cut the track between the NE567 pin 7 and RV1. The TU circuit diagram needs amending too.

- The TU input goes to bit ONE of the PIO port A, as in the diagram, and not to bit ZERO as on early PCB's. Move the link if necessary.

- The clock input to the PIO has been omitted from the circuit diagram, but the PCB is OK. PIO pin 25 should go to Z80A pin 6. The PIO should be a Z80A PIO, the 4MHz version.

	SW8	SW7	SW6	SW5	SW4	SW3	SW2	SW1
SWITCH FUNCTIONS			ASCII BAUD RATE	CLOCK FREQ 0 = 3.579 1 = 4.000			OPEN TU INPUT	SPARE
	MODE		0 = 110 1 = 300		RTTY BAUD RATE			
CLOSED = '0'	00 = MORSE				00 = 45			
OPEN = '1'	01 = RTTY				01 = 50			
SW2 ALWAYS OPEN	10 = ASCII				10 = 56			
	11 = SPARE				11 = 75			

Table 1 The switch functions.